



Analog IC Design

Lecture 02 Review on Circuits Basics

Dr. Hesham A. Omran

Integrated Circuits Lab (ICL)
Electronics and Communications Eng. Dept.
Faculty of Engineering
Ain Shams University

Ohm's Law

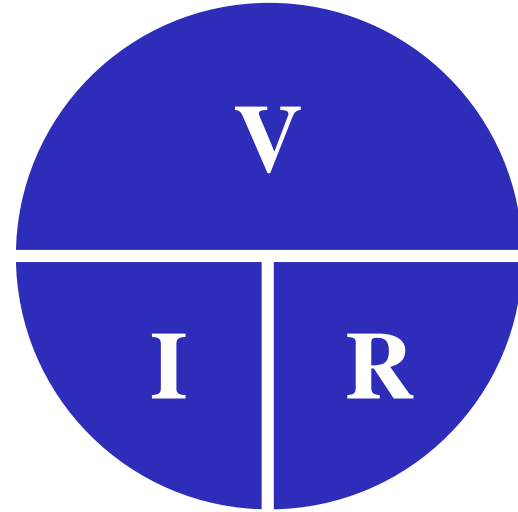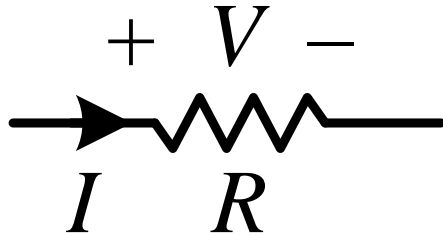

$$V = IR$$

$$I = \frac{V}{R}$$


$$R = \frac{V}{I}$$

Kirchhoff's Current Law (KCL)

- ❑ The sum of all currents flowing into a node is zero.

$$\Sigma I = 0$$

$$I_1 + I_2 + I_3 - I_4 = 0$$

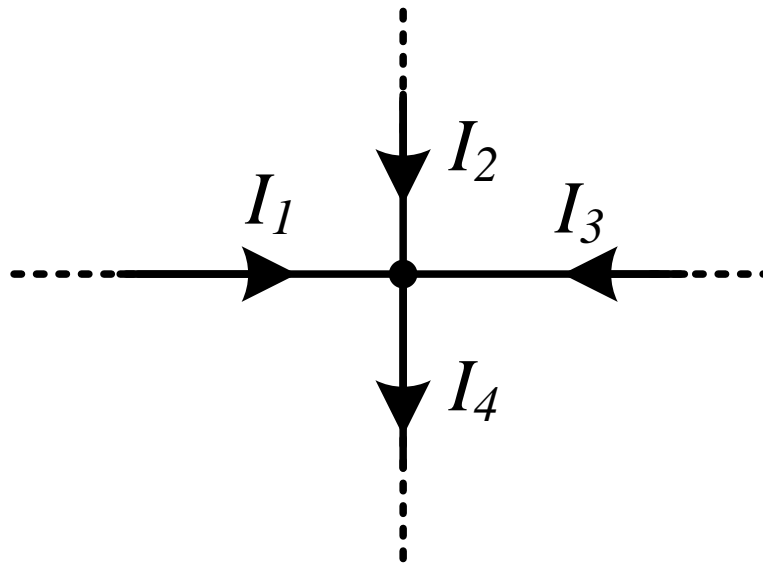


Kirchhoff's Voltage Law (KVL)

- The sum of all voltage drops around any closed loop is zero

$$\Sigma V = 0$$

$$-V_{DD} + I_D R_D + V_{DS} + I_D R_S = 0$$

$$V_{DD} = I_D (R_D + R_S) + V_{DS}$$

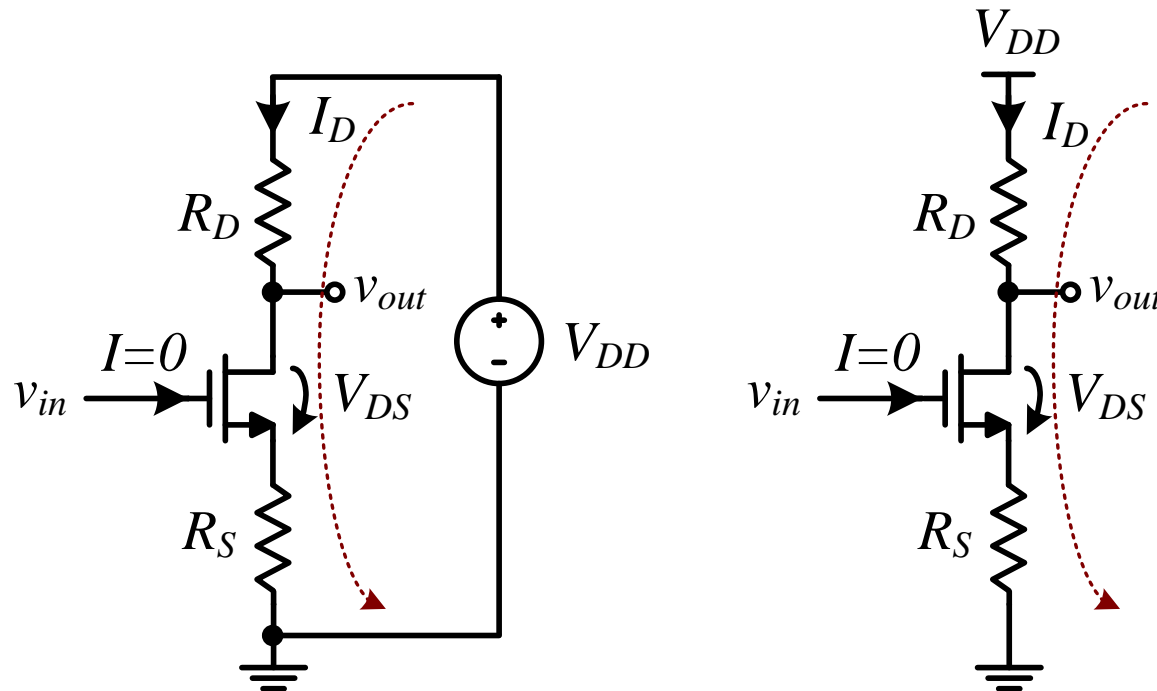


Resistor Combinations

- Resistors in series: Largest resistor dominates



$$R_{eq} = R_1 + R_2 + R_3$$

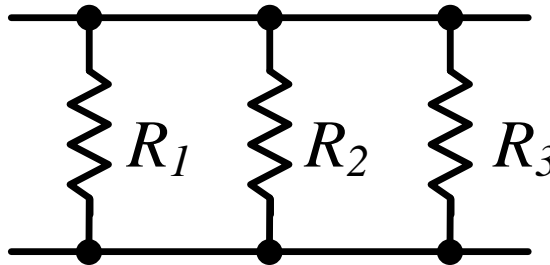- Resistors in parallel: Smallest resistor dominates





$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Voltage and Current Dividers

- ❑ Voltage divider → the largest resistor takes most of the voltage
- ❑ Current divider → the smallest resistor (largest conductance) takes most of the current
 - Remember that current flows in the least resistance path

$$V_{out} = V_{DD} \cdot \frac{R_3}{R_1 + R_2 + R_3}$$
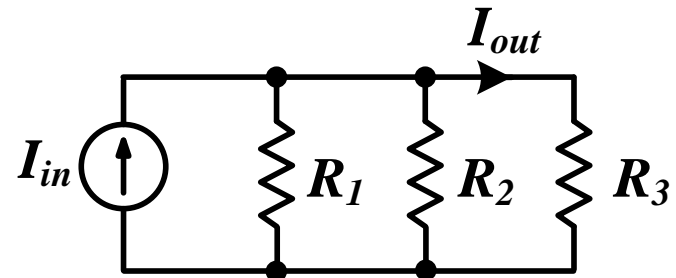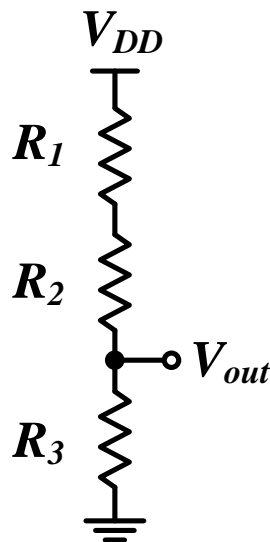
$$I_{out} = I_{in} \cdot \frac{G_3}{G_1 + G_2 + G_3}$$




Thevenin Equivalent Circuit

- Any one port circuit can be replaced by a voltage source and a series impedance

$$V_{TH} = V_{o.c.}$$
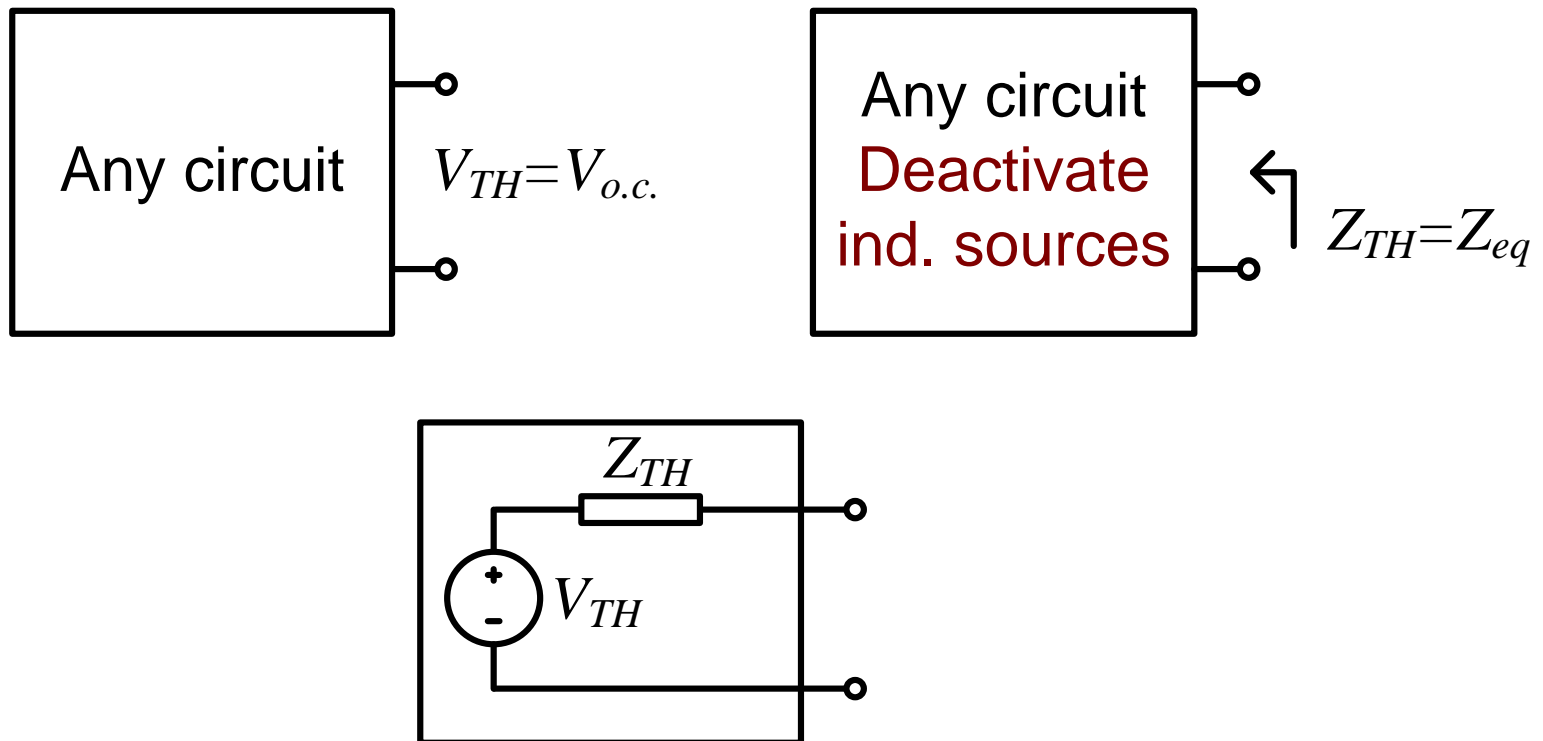
$$Z_{TH} = Z_{eq} \text{ (turn OFF all independent sources)}$$



Norton Equivalent Circuit


- Any one port circuit can be replaced by a current source and a parallel impedance

$$I_N = I_{s.c.}$$

$$Z_N = Z_{eq} \text{ (turn OFF all independent sources)}$$

$$Z_N = Z_{TH}$$

$$V_{TH} = V_{o.c.} = I_N \times Z_N$$

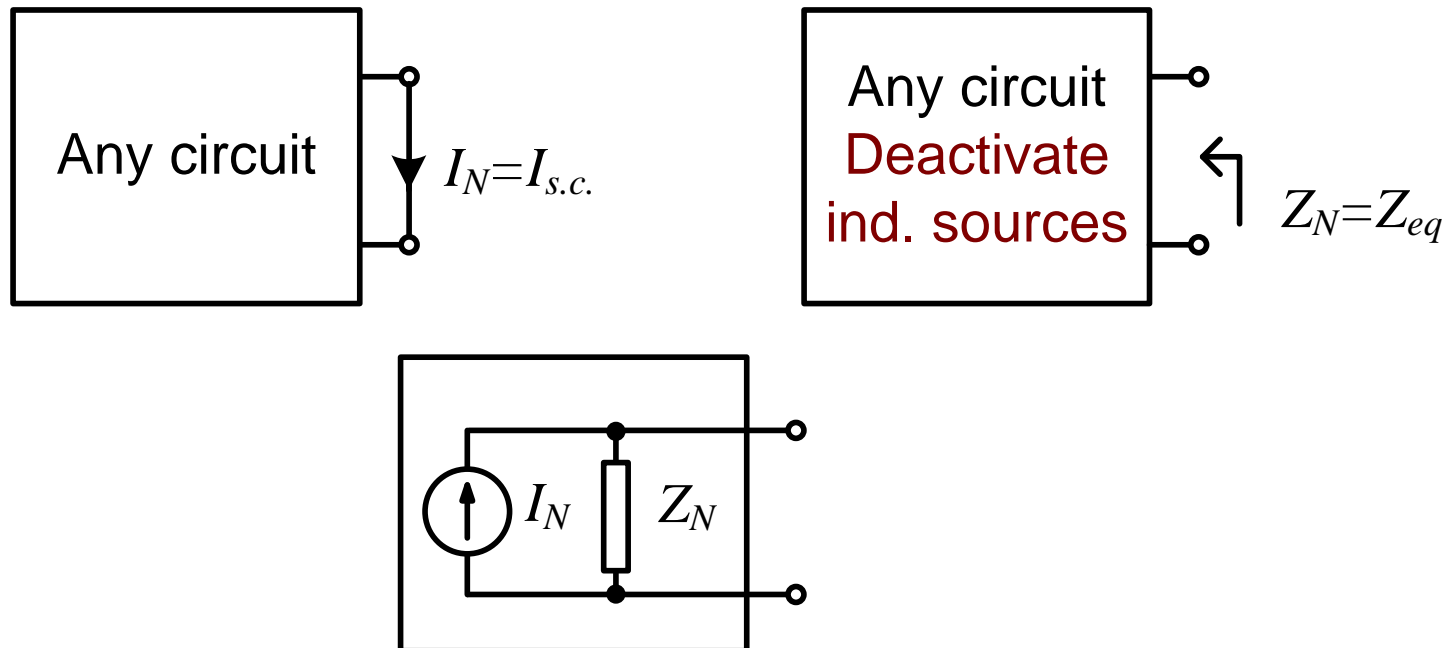

Superposition Theorem

- ❑ Deactivate all independent sources except one
 - Independent voltage source \rightarrow short circuit (s.c.)
 - Independent current source \rightarrow open circuit (o.c.)
 - Do NOT deactivate dependent sources
- ❑ Solve the circuit
- ❑ Repeat the previous two steps for every source
- ❑ Algebraically add all the results

We use this frequently to separate AC and DC solutions

Superposition Theorem




DC + AC

=

DC

+

AC

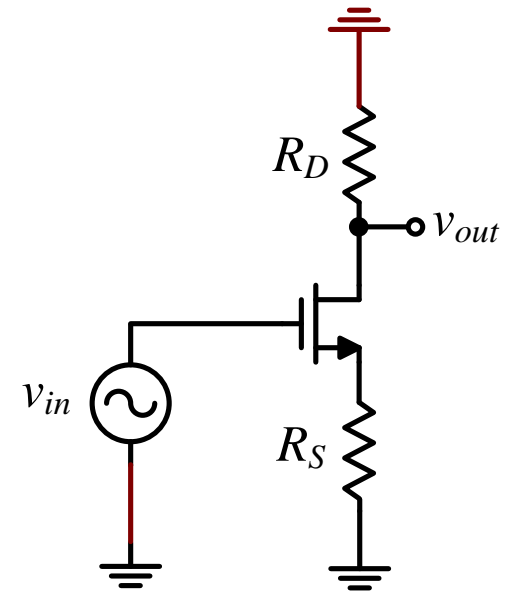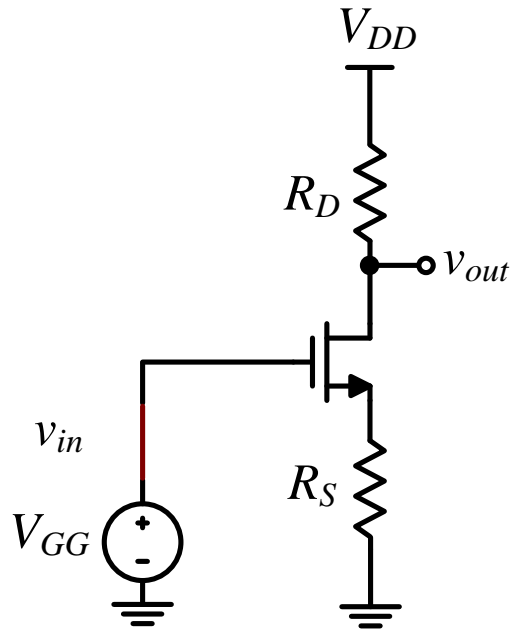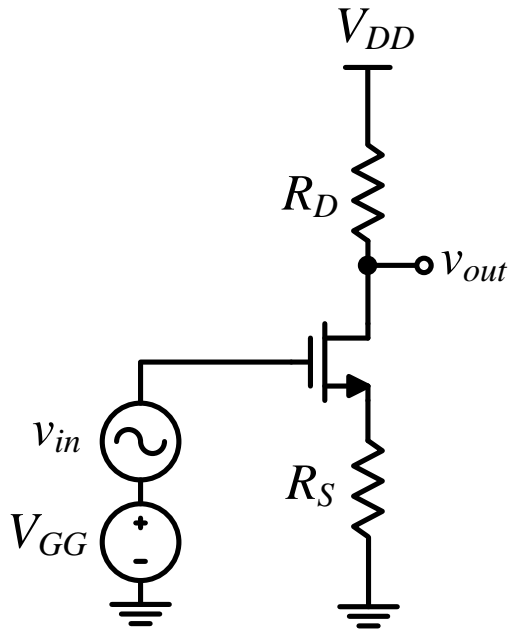

Capacitance

$$Q = CV$$

$$i = \frac{dQ}{dt} = C \frac{dV}{dt}$$

$$V = V_o \cos \omega t = V_o \cdot \operatorname{Re}\{e^{j\omega t}\} \Rightarrow V_o e^{j\omega t}$$

$$i = C \frac{dV}{dt} = j\omega C (V_o e^{j\omega t}) = j\omega C \cdot V$$


$$Z_C = \frac{V}{i} = \frac{1}{j\omega C} = \frac{1}{sC} \Rightarrow X_C = \frac{1}{\omega C}$$

$$\omega \uparrow\uparrow \Rightarrow X_C \rightarrow 0 \Rightarrow s.c.$$

$$\omega \downarrow\downarrow \Rightarrow X_C \rightarrow \infty \Rightarrow o.c.$$


Capacitance Combinations

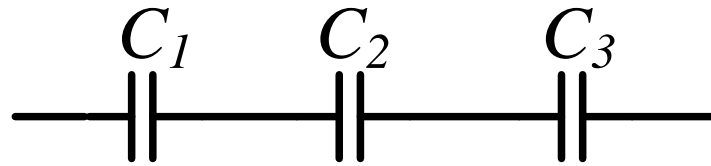- ❑ Capacitors in series: Smallest capacitor dominates




$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

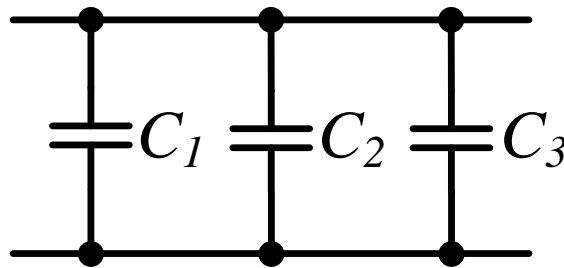- ❑ Capacitors in parallel: Largest capacitor dominates



$$C_{eq} = C_1 + C_2 + C_3$$

Laplace Transform (LT)

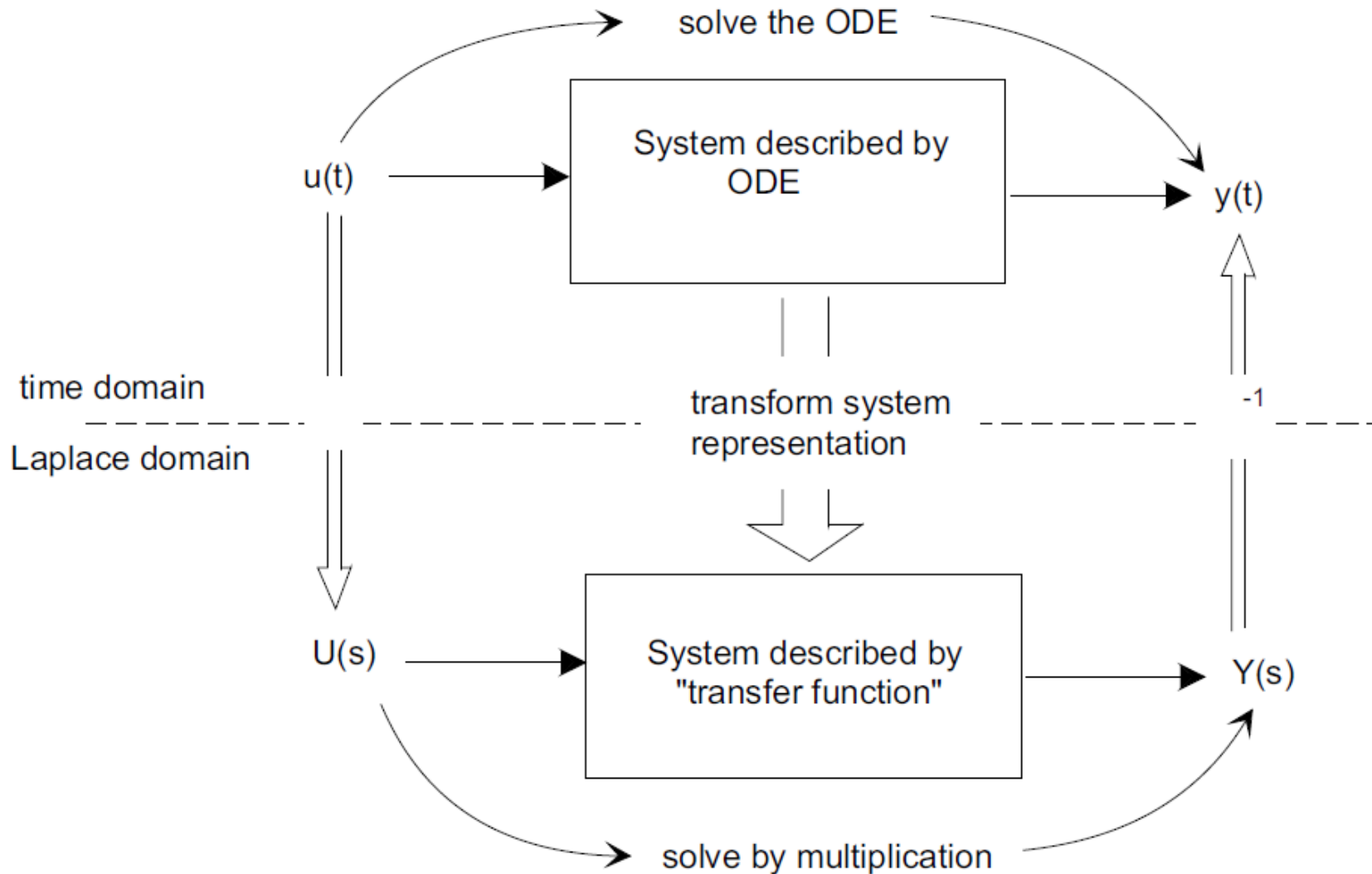

Poles and Zeros

Transfer function

$$H(s) = \frac{N(s)}{D(s)}$$


Zeros: roots of the numerator $\rightarrow N(s) = 0$

Poles: roots of the denominator (characteristic eq.) $\rightarrow D(s) = 0$

For physical systems, poles & zeros are real or complex conjugate

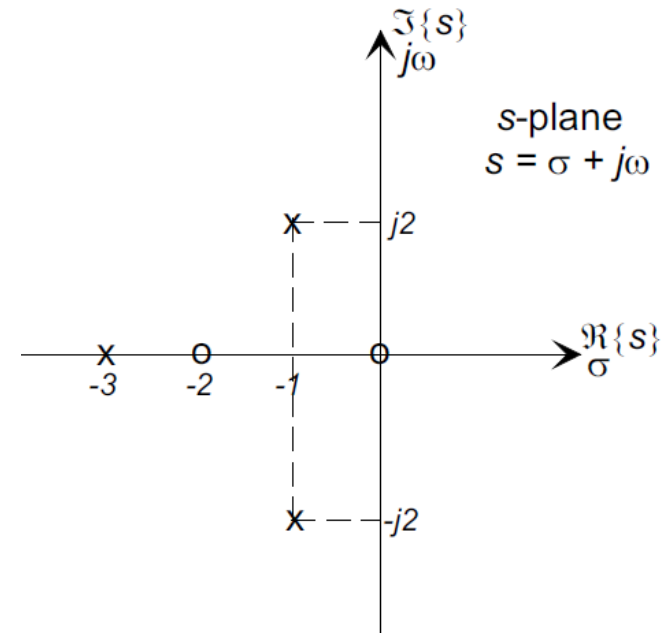
Example:

$$\begin{aligned} G(s) &= \frac{5s^2 + 10s}{s^3 + 5s^2 + 11s + 5} \\ &= \frac{5s(s + 2)}{(s + 3)(s^2 + 2s + 5)} \\ &= \frac{5s(s + 2)}{(s + 3)(s + (1 + j2))(s + (1 - j2))} \end{aligned}$$



Pole-Zero Plot

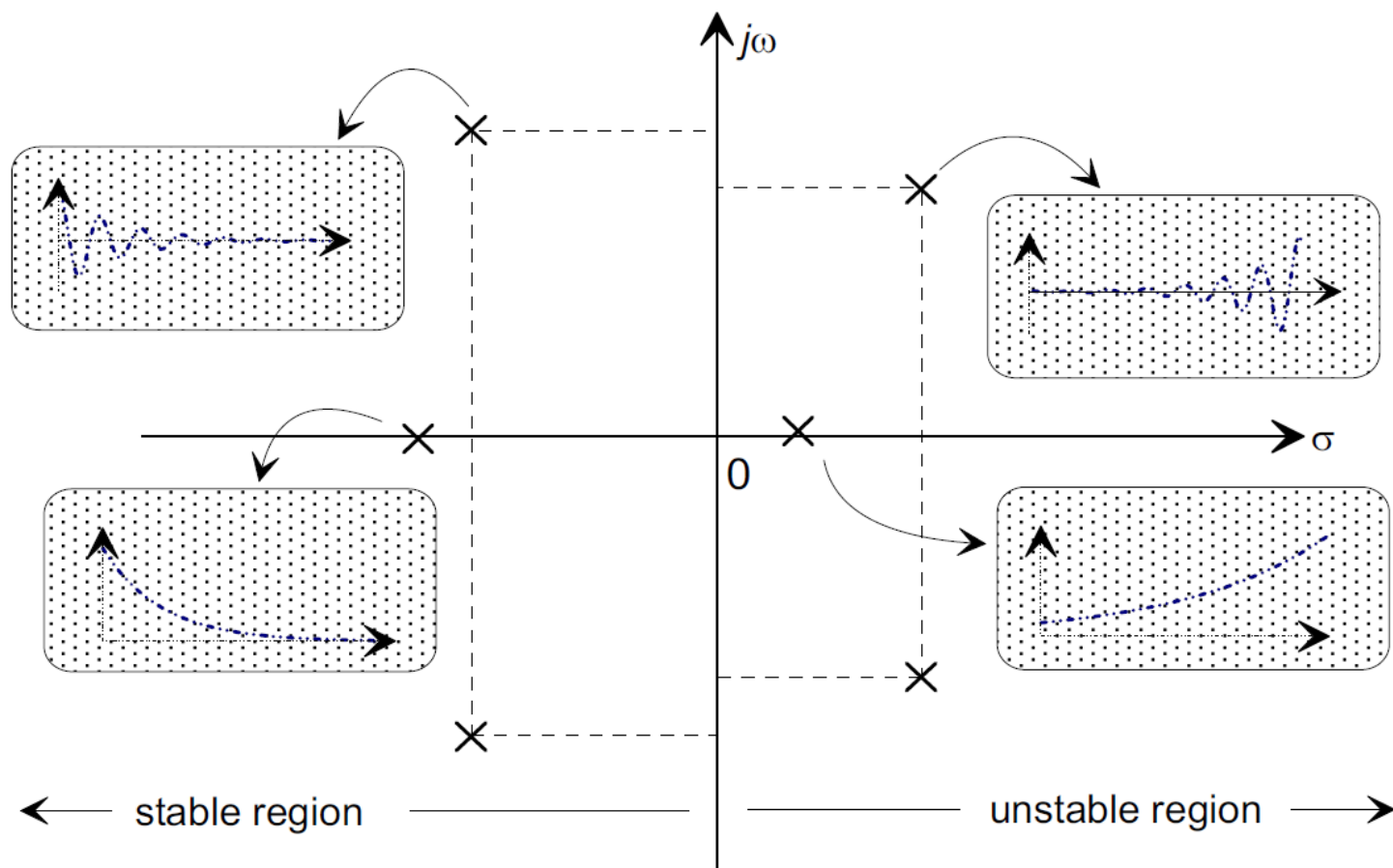- ❑ Poles in LHP: Decaying exponential → Stable system
 - BIBO: Bounded input bounded output
- ❑ Poles in RHP: Growing exponential → Unstable system



Frequency Response

- ❑ Transfer function

$$H(s) = \frac{N(s)}{D(s)}$$


- ❑ Fourier Transform is a special case of Laplace Transform: $s \Rightarrow j\omega$
 - $\sigma = 0 \rightarrow$ Steady state response for sinusoidal input
- ❑ Transfer function \rightarrow Frequency response: $s \Rightarrow j\omega$

$$H(j\omega) = \frac{V_{out}(j\omega)}{V_{in}(j\omega)} = |H(j\omega)|e^{j\phi}$$

- ❑ $a + jb = re^{j\theta}$

- ❑ $r = \text{Magnitude}(a + jb) = \sqrt{a^2 + b^2}$


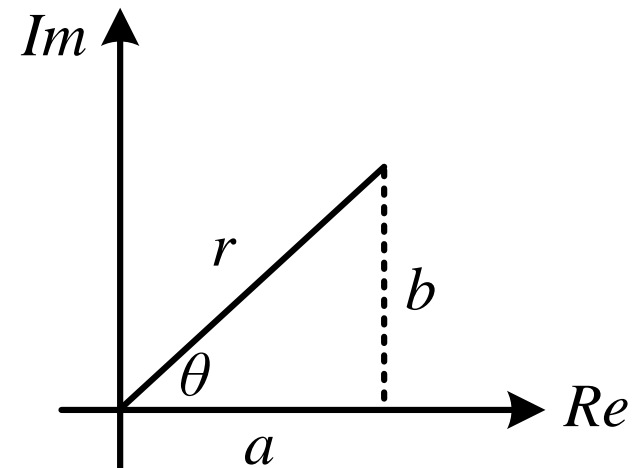
- ❑ $\theta = \text{Phase}(a + jb) = \tan^{-1} \frac{b}{a}$





Frequency Response

□ Y-axis: magnitude of frequency response, x-axis: frequency



LPF

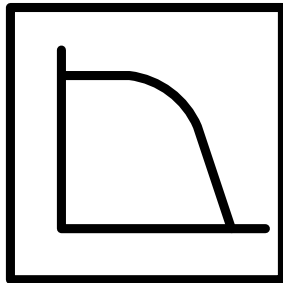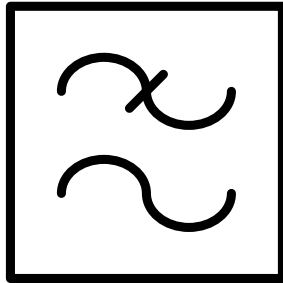

BPF

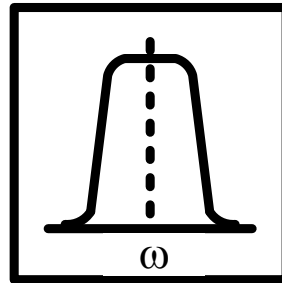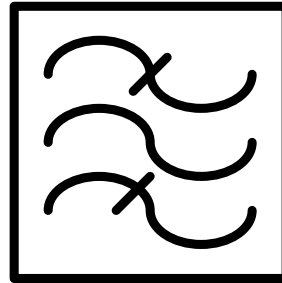

HPF

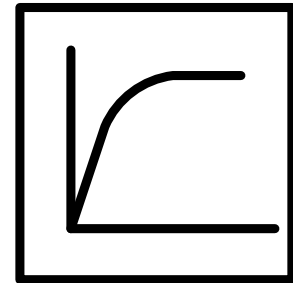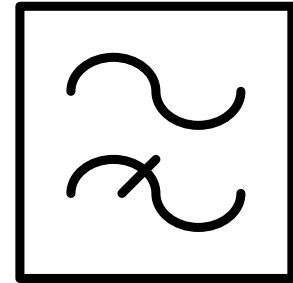

1st Order LPF

$$H(s) = \frac{v_{out}(s)}{v_{in}(s)} = \frac{1/sC}{R + 1/sC} = \frac{1}{1 + sRC} = \frac{1}{1 + s\tau}$$
$$H(j\omega) = \frac{v_{out}(j\omega)}{v_{in}(j\omega)} = \frac{1/j\omega C}{R + 1/j\omega C} = \frac{1}{1 + j\omega RC} = \frac{1}{1 + \frac{j\omega}{\omega_c}}$$

□ $\tau = RC$: time constant



□ $\omega_c = \frac{1}{\tau} = \frac{1}{RC}$: cutoff/corner frequency

□ Poles: $s_p = -\frac{1}{\tau} = -\omega_c$

□ Zeros: ?

□ $|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}}$

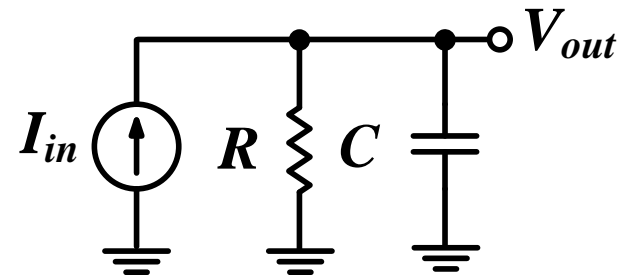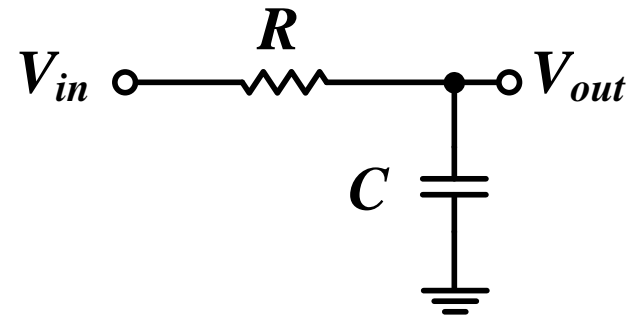□ $P(H(j\omega)) = -\tan^{-1} \frac{\omega}{\omega_c}$



Bode Plot Rules


	Pole	Zero
Magnitude	-20 dB/decade Actual Mag @ pole: -3 dB	+20 dB/decade Actual Mag @ zero: +3 dB
Phase	-90° Actual Phase @ pole: -45°	LHP zero: +90° Actual Phase @ zero: +45° RHP zero: -90° Actual Phase @ zero: -45°

→ RHP: Right-half plane ($\text{Re}\{s\} > 0$)

→ LHP: Left-half plane ($\text{Re}\{s\} < 0$)


1st Order LPF Bode Plot

$20 \log|H(j\omega)|$ (dB)

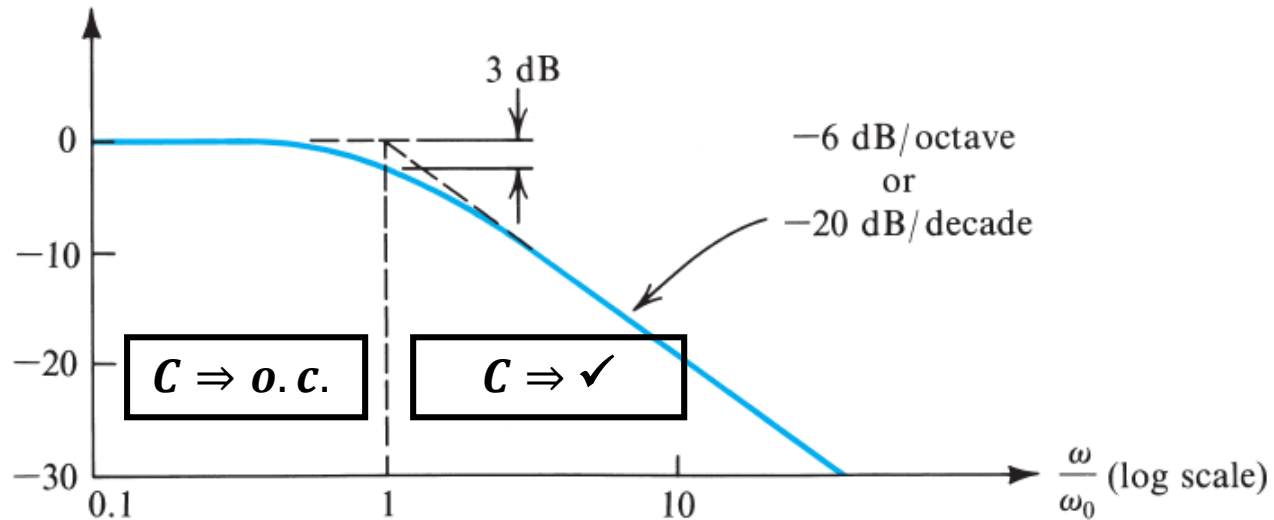

(a)

$P(H(j\omega))$

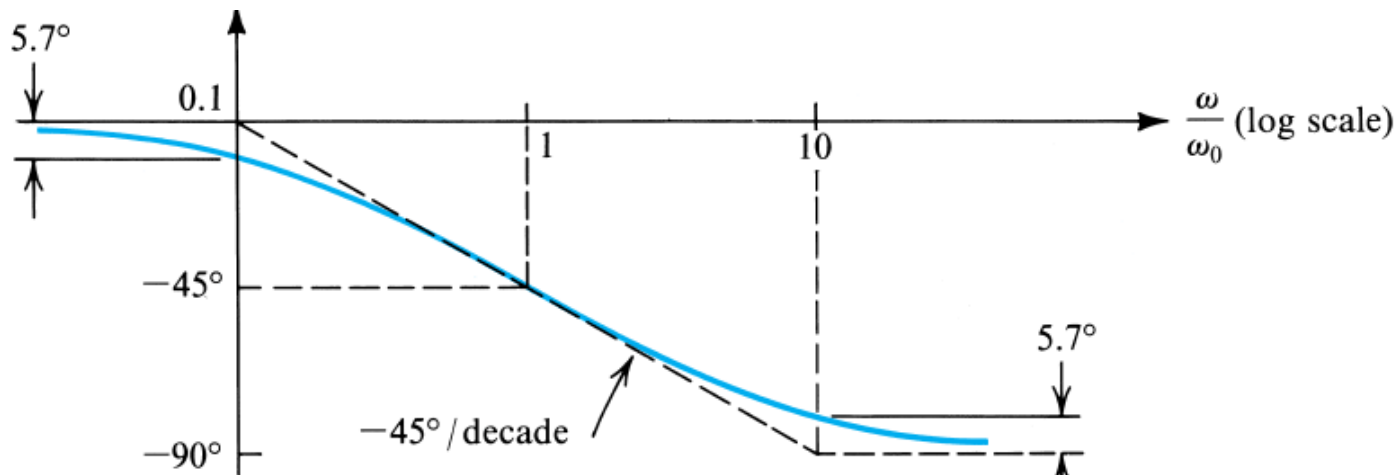

(b)

1st Order HPF

$$H(s) = \frac{v_{out}(s)}{v_{in}(s)} = \frac{R}{R + 1/sC} = \frac{sRC}{1 + sRC} = \frac{s\tau}{1 + s\tau}$$


$$H(j\omega) = \frac{v_{out}(j\omega)}{v_{in}(j\omega)} = \frac{R}{R + 1/j\omega C} = \frac{j\omega RC}{1 + j\omega RC} = \frac{\frac{j\omega}{\omega_c}}{1 + \frac{j\omega}{\omega_c}}$$

❑ Poles: $s_p = -\frac{1}{\tau} = -\omega_c$

❑ Zeros: $s_z = 0$

❑ $|H(j\omega)| = \frac{\frac{\omega}{\omega_c}}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}}$

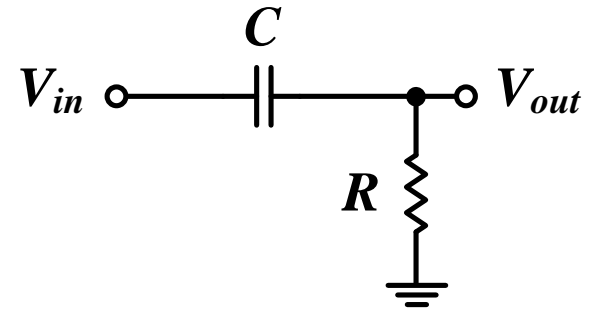❑ $P(H(j\omega)) = 90^\circ - \tan^{-1} \frac{\omega}{\omega_c}$




Bode Plot Rules

	Pole	Zero
Magnitude	-20 dB/decade Actual Mag @ pole: -3 dB	+20 dB/decade Actual Mag @ zero: +3 dB
Phase	-90° Actual Phase @ pole: -45°	LHP zero: +90° Actual Phase @ zero: +45° RHP zero: -90° Actual Phase @ zero: -45°


- RHP: Right-half plane ($\text{Re}\{s\} > 0$)
- LHP: Left-half plane ($\text{Re}\{s\} < 0$)

1st Order HPF Bode Plot

$20 \log|H(j\omega)|$ (dB)

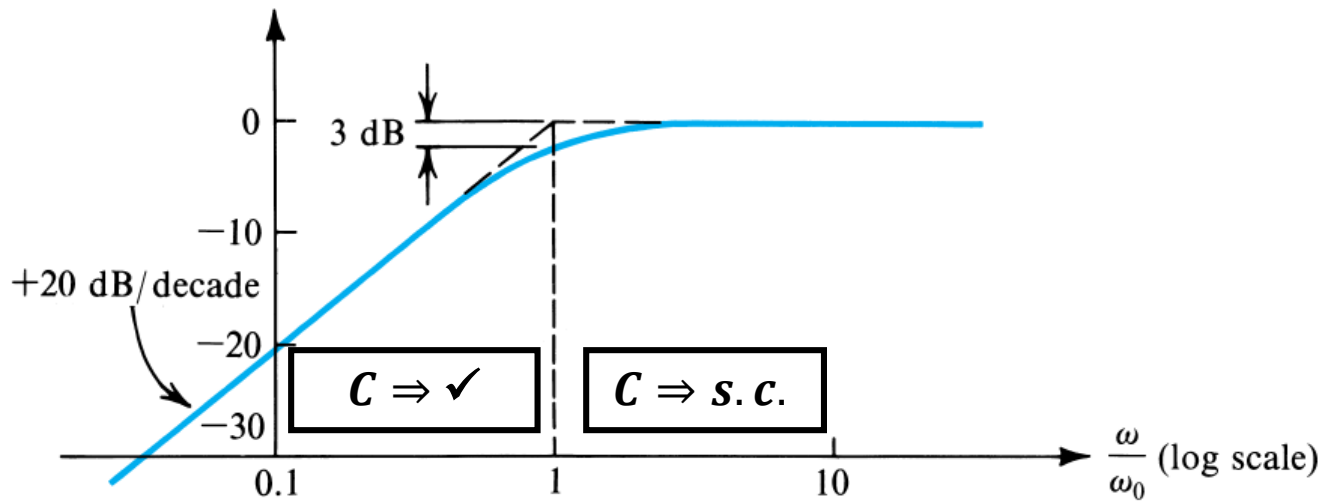

(a)

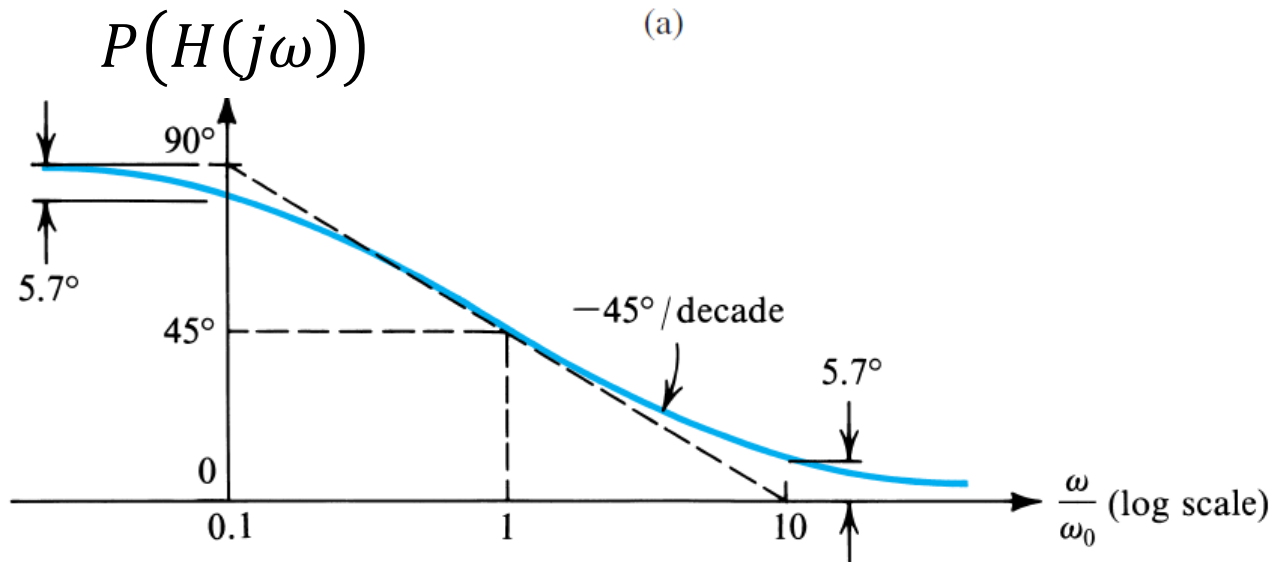

(b)

References

- ❑ T. Floyd and D. Buchla, “Electronics Fundamentals, Circuits, Devices, and Applications,” 8th ed., Pearson, 2014
- ❑ A. Sedra and K. Smith, “Microelectronic circuits,” Oxford University Press, 7th ed., 2015
- ❑ B. Razavi, “Fundamentals of microelectronics,” 2nd ed., Wiley, 2014

Thank you!